



# Summary

## Module II (10 Hours)


Sequential circuit - Clocking, Flip flops - SR – JK- D -T flip flops, Counters - Synchronous and asynchronous counters - UP/DOWN counters , Registers - Serial in serial out - Serial in parallel out - Parallel in serial out - Parallel in parallel out registers

# Summary
 
## Latches

A **latch** is a temporary storage device that has two stable states (bistable). It is a **basic form of memory**.

The **S-R (Set-Reset) latch** is the most basic type. It can be constructed from NOR gates or NAND gates. With NOR gates, the latch responds to active-HIGH inputs; with NAND gates, it responds to active-LOW inputs.



NOR Active-HIGH Latch


# Summary

## Latches

The **active-HIGH S-R latch** is in a stable (latched) condition when both inputs are LOW.

Assume the latch is initially RESET ( $Q = 0$ ) and the inputs are at their inactive level (0). To SET the latch ( $Q = 1$ ), a momentary **HIGH** signal is applied to the  $S$  input while the  $R$  remains LOW.

 To RESET the latch ( $Q = 0$ ), a momentary **HIGH** signal is applied to the  $R$  input while the  $S$  remains LOW.



# Summary


## Latches

The **active-LOW  $\overline{S}$ - $\overline{R}$  latch** is in a stable (latched) condition when both inputs are HIGH.

Assume the latch is initially RESET ( $Q = 0$ ) and the inputs are at their inactive level (1). To SET the latch ( $Q = 1$ ), a momentary **LOW signal** is applied to the  $\overline{S}$  input while the  $\overline{R}$  remains HIGH.

To RESET the latch a momentary **LOW** is applied to the  $\overline{R}$  input while  $\overline{S}$  is HIGH.

 
Never apply an active set and reset at the same time (invalid).



# S-R Latch


- Characteristics table for active-high input S-R latch:

S	R	Q	Q'	
0	0	NC	NC	No change. Latch remained in present state.
1	0	1	0	Latch SET.
0	1	0	1	Latch RESET.
1	1	0	0	Invalid condition.

 

- Characteristics table for active-low input S'-R' latch:

S'	R'	Q	Q'	
1	1	NC	NC	No change. Latch remained in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition.

 

# Summary

## Latches



A **gated latch** is a variation on the basic latch.

The gated latch has an additional input, called enable ( $EN$ ) that must be HIGH in order for the latch to respond to the  $S$  and  $R$  inputs.

  **Example** Show the  $Q$  output with relation to the input signals.

Assume  $Q$  starts LOW.


**Solution** Keep in mind that  $S$  and  $R$  are only active when  $EN$  is HIGH.



# Summary
 
## Latches

The ***D* latch** is an variation of the *S-R* latch but combines the *S* and *R* inputs into a single *D* input as shown:



A simple rule for the *D* latch is:

***Q* follows *D* when the Enable is active.**

# Summary

## Latches

The truth table for the  $D$  latch summarizes its operation. If  $EN$  is LOW, then there is no change in the output and it is latched.

Inputs		Outputs		Comments
$D$	$EN$	$Q$	$\bar{Q}$	
0	1	0	1	RESET
1	1	1	0	SET
X	0	$Q_0$	$\bar{Q}_0$	No change

$C$	$D$	$Q$
0	x	No change
1	0	0
1	1	1





# Summary

## Latches
  
### Example

Determine the  $Q$  output for the  $D$  latch, given the inputs shown.




Notice that the Enable is not active during these times, so the **output is latched**.

# Summary
 
## Flip-flops

A flip-flop differs from a latch **in the manner it changes states**. A flip-flop is a **clocked device**, in which only the clock edge determines when a new bit is entered.

The active edge can be positive or negative.



# FF vs. Latch

- **Latches and flip-flops** (FFs) are the basic building blocks of sequential circuits.
  - latch: bistable memory device with level sensitive triggering (no clock), **watches all of its inputs continuously and changes its outputs, independent of a clocking signal.**
  - flip-flop: bistable memory device with edge-triggering (with clock), **samples its inputs, and changes its output only at times determined by a clocking signal.**

# Summary

## Flip-flops


The truth table for a **positive-edge triggered D flip-flop** shows an up arrow to remind you that **it is sensitive to its  $D$  input only on the rising edge of the clock**; otherwise it is latched. The truth table for a **negative-edge triggered D flip-flop** is identical except for the direction of the arrow.

Inputs		Outputs		Comments
$D$	CLK	$Q$	$\bar{Q}$	
1	↑	1	0	SET
0	↑	0	1	RESET

(a) Positive-edge triggered

Inputs		Outputs		Comments
$D$	CLK	$Q$	$\bar{Q}$	
1	↓	1	0	SET
0	↓	0	1	RESET

(b) Negative-edge triggered

 


# Summary

## Flip-flops


The **J-K flip-flop** is more versatile than the D flip flop. In addition to the clock input, it has two inputs, labeled  $J$  and  $K$ . When both  $J$  and  $K = 1$ , the output changes states (**toggles**) on the active clock edge (in this case, the rising edge).

Inputs			Outputs		Comments
$J$	$K$	CLK	$Q$	$\bar{Q}$	
0	0	↑	$Q_0$	$\bar{Q}_0$	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\bar{Q}_0$	$Q_0$	Toggle

# JK Flip-Flop

 

(a) Logic diagram

 

(b) Graphical symbol

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

(c) Transition table

C	J	K	$Q_{\text{next}}$
0	x	x	No change
1	0	0	No change
1	0	1	0 (reset)
1	1	0	1 (set)
1	1	1	$Q'_{\text{current}}$

Clocked JK flip-flop


# Summary

## Flip-flops

 
### Example

Determine the  $Q$  output for the  $J$ - $K$  flip-flop, given the inputs shown.


Notice that the **outputs change on the leading edge of the clock.**




### Solution

 

# T Flip-Flop

 

(a) Logic diagram

 


(b) Graphical symbol

Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

(c) Transition table

Clocked T flip-flop

 

C	T	Q <sub>next</sub>
0	x	No change
1	0	No change
1	1	Q' <sub>current</sub>




# Summary
 
## Flip-flops

A D-flip-flop does not have a toggle mode like the J-K flip-flop, but you can hardwire a toggle mode by connecting  $\bar{Q}$  back to  $D$  as shown. This is useful in some counters.

For example, if  $Q$  is LOW,  $\bar{Q}$  is HIGH and the flip-flop will toggle on the next clock edge. Because the flip-flop only changes on the active edge, the output will only change once for each clock pulse.




D flip-flop hardwired for a toggle mode

# Summary
 
## Flip-flops

*Synchronous* inputs are transferred in the triggering edge of the **clock** (for example the *D* or *J-K* inputs). Most flip-flops have other inputs that are *asynchronous*, meaning they affect the output **independent of the clock**.

Two such inputs are normally labeled preset (*PRE*) and clear (*CLR*). These inputs are usually **active LOW**. A J-K flip flop with active LOW preset and CLR is shown.





# Summary

## Flip-flops

### Example

Determine the  $Q$  output for the  $J$ - $K$  flip-flop, given the inputs shown.


### Solution

 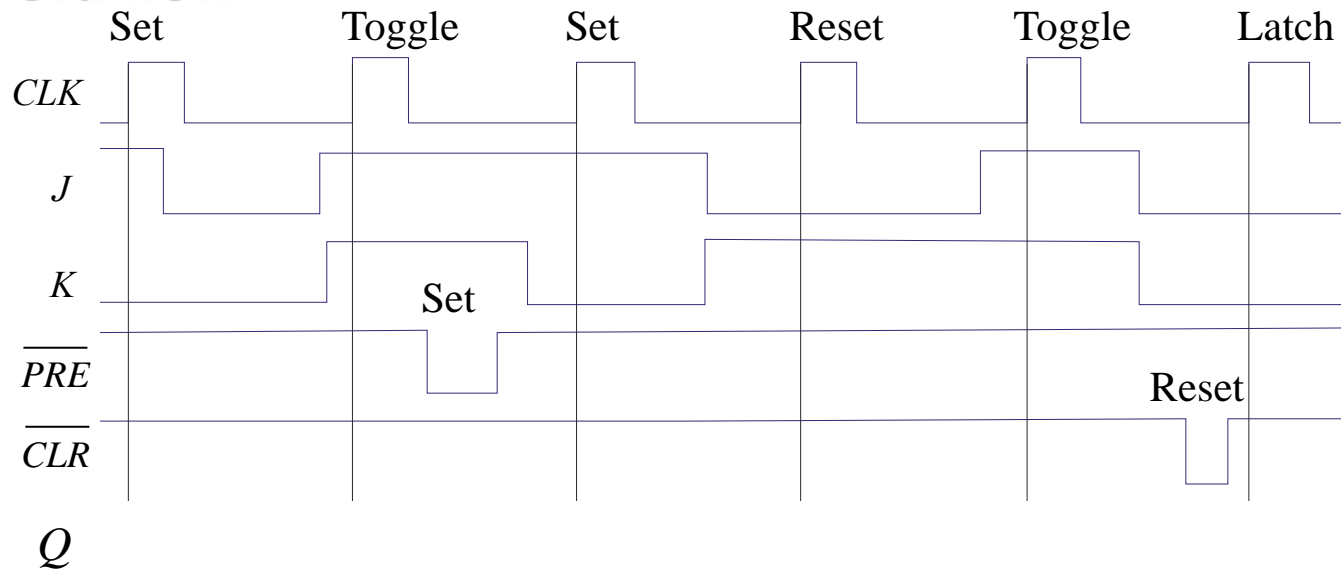

# Summary
 
## Flip-flop Characteristics


**Propagation delay time** is specified for the **rising and falling outputs**. It is measured between the 50% level of the **clock** to the 50% level of the **output transition**.



# Summary
 
## Flip-flop Characteristics

Another **propagation delay time** specification is the time required for an *asynchronous* input to cause a change in the output. Again it is measured from the 50% levels.




# Summary

 
## Flip-flop Characteristics

**Set-up time** and **hold time** are times required before and after the clock transition that data must be present to be reliably clocked into the flip-flop.

**Setup time** is the minimum time for the data to be present *before* the clock.



 **Hold time** is the minimum time for the data to *remain* after the clock.





# Summary

## Flip-flop Characteristics

Other specifications include **maximum clock frequency**, **minimum pulse widths for various inputs**, and **power dissipation**. The **power dissipation** is the product of the supply voltage and the average current required.


A useful comparison between logic families is the **speed-power product** which uses two of the specifications discussed: the average propagation delay and the average power dissipation. The unit is energy.

# Summary
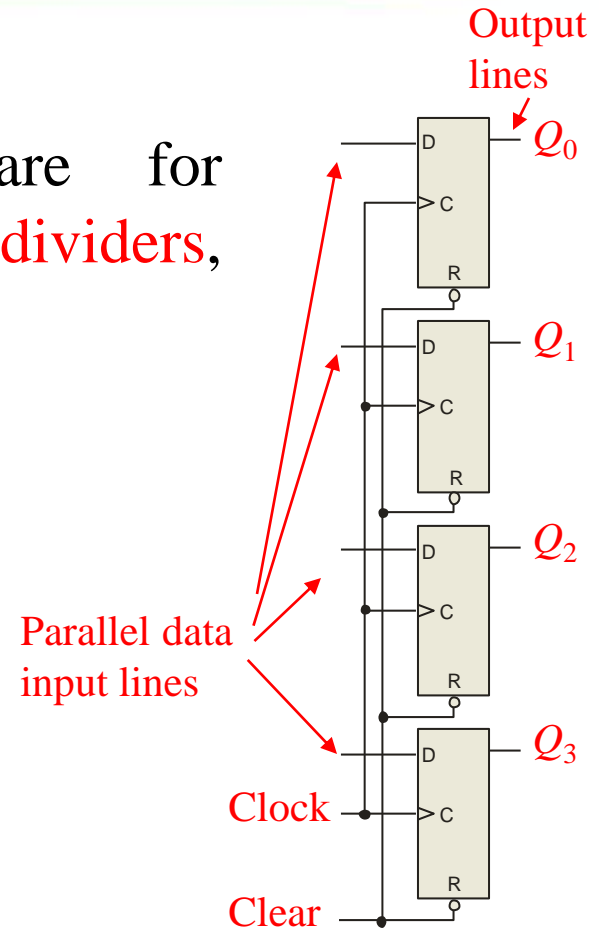
## Flip-flop Applications

Principal flip-flop applications are for **temporary data storage**, as **frequency dividers**, and in **counters**

Typically, for **data storage** applications, a group of flip-flops are connected to **parallel** data lines and clocked together. Data is stored until the next clock pulse.






# Summary

 
## Flip-flop Applications

For **frequency division**, it is simple to use a flip-flop in the **toggle mode** or to chain a series of toggle flip flops to continue to divide by two.

One flip-flop will divide  $f_{in}$  by 2, two flip-flops will divide  $f_{in}$  by 4 (and so on).




Waveforms:

 


# T Flip-flop

- Application: *Frequency division.*

 

Divide clock frequency by 2.

 

Divide clock frequency by 4.

- Application: *Counter*

# Selected Key Terms

***Latch*** A bistable digital circuit used for storing a bit.

***Bistable*** Having two stable states. Latches and flip-flops are bistable multivibrators.

***Clock*** A triggering input of a flip-flop.

***D flip-flop*** A type of bistable multivibrator in which the output assumes the state of the *D* input on the triggering edge of a clock pulse.

***J-K flip-flop*** A type of flip-flop that can operate in the SET, RESET, no-change, and toggle modes.



## Selected Key Terms

- Propagation delay time*** The interval of time required after an input signal has been applied for the resulting output signal to change.
- Set-up time*** The time interval required for the input levels to be on a digital circuit.
- Hold time*** The time interval required for the input levels to remain steady to a flip-flop after the triggering edge in order to reliably activate the device.



# Summary

## Module II (10 Hours)

Sequential circuit - Clocking, Flip flops - SR – JK- D -T flip flops, **Counters - Synchronous and asynchronous counters - UP/DOWN counters** , Registers - Serial in serial out - Serial in parallel out - Parallel in serial out - Parallel in parallel out registers

## Counting in Binary

As you know, the binary count sequence follows a familiar pattern of 0's and 1's

The next bit changes on every fourth number.


0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

LSB changes on every number.

The next bit changes on every 2<sup>ND</sup> number.
 
## Counting in Binary

A counter can form the same pattern of 0's and 1's with logic levels. The first stage in the counter represents the least significant bit – notice that these waveforms follow the same pattern as counting in binary.



# Introduction: Counters

- **Counters** are circuits that cycle through a specified number of states.
- Two types of counters:
  - ❖ synchronous (parallel) counters
  - ❖ asynchronous (ripple) counters
- Ripple counters allow **some flip-flop outputs to be used as a source of clock** for other flip-flops.(do not have common clock pulse).
- Synchronous counters **apply the same clock to all flip-flops.**




# Asynchronous (Ripple) Counters

- **Asynchronous counters:** the flip-flops do not change states at exactly the same time as they do not have a common clock pulse.
- Also known as **ripple counters**, as the input clock pulse “ripples” through the counter – **cumulative delay** is a drawback.
- $n$  flip-flops  $\rightarrow$  a MOD (modulus)  $2^n$  counter.
- Output of the last flip-flop (MSB) divides the input clock frequency by the MOD number of the counter, hence a counter is also a *frequency divider*.


# Asynchronous (Ripple) Counters

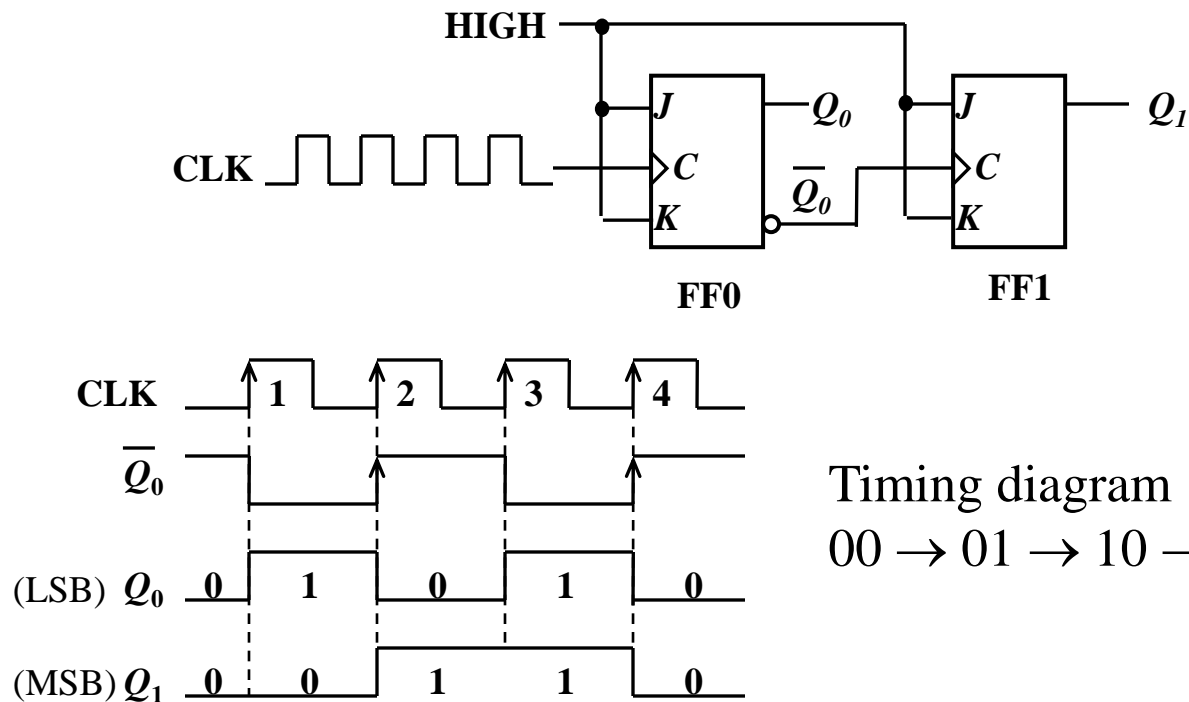- Example: **2-bit ripple(asynchronous) binary counter**
- Clock is connected to the clock input of only the first flipflop.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.



# Asynchronous (Ripple) Counters


- Example: 3-bit ripple binary counter

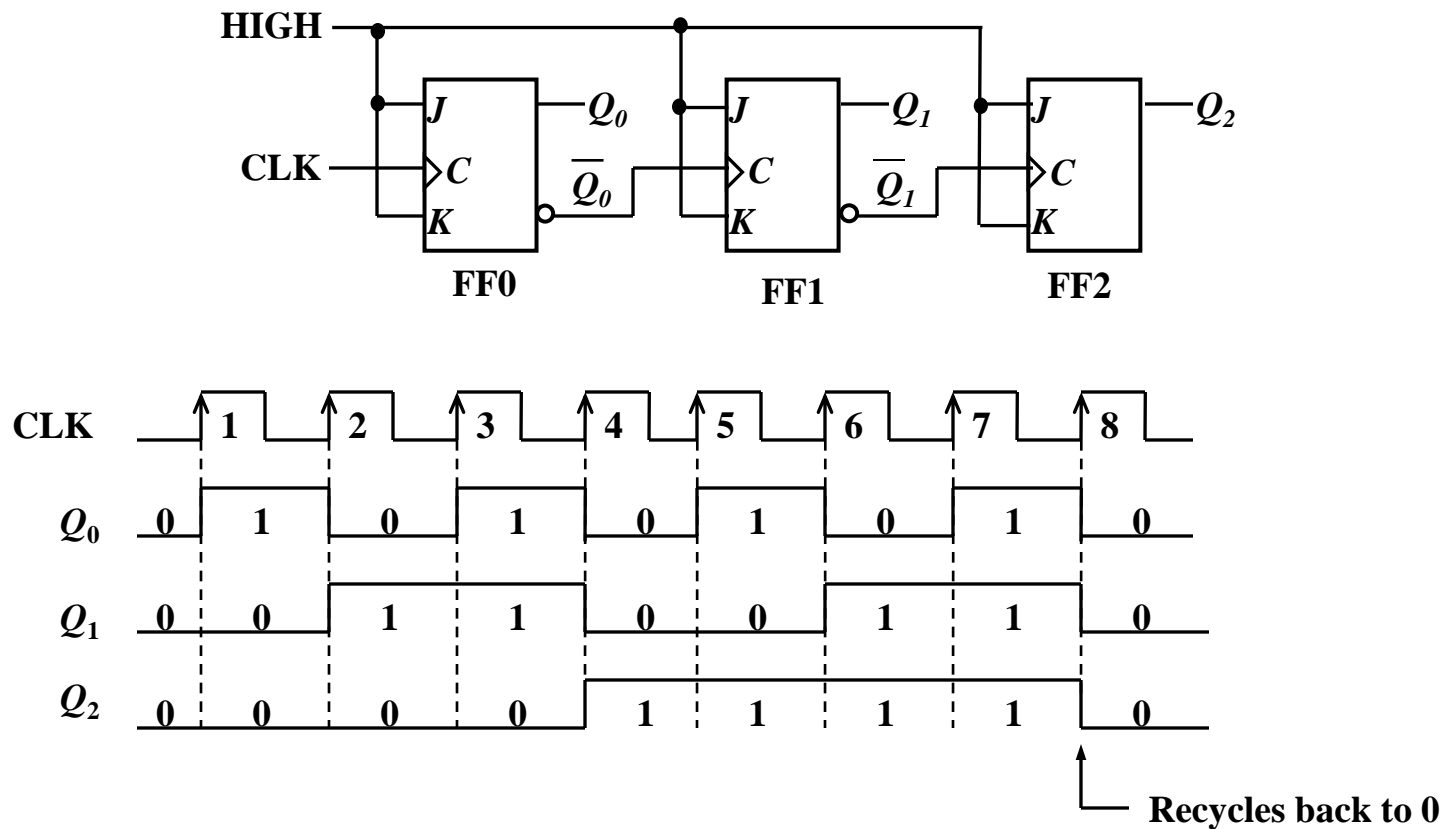
 
## Three bit Asynchronous Counter


In an asynchronous counter, the clock is applied only to the first stage. Subsequent stages derive the clock from the previous stage.

The three-bit asynchronous counter shown is typical. It uses J-K flip-flops in the toggle mode.




# Asynchronous (Ripple) Counters

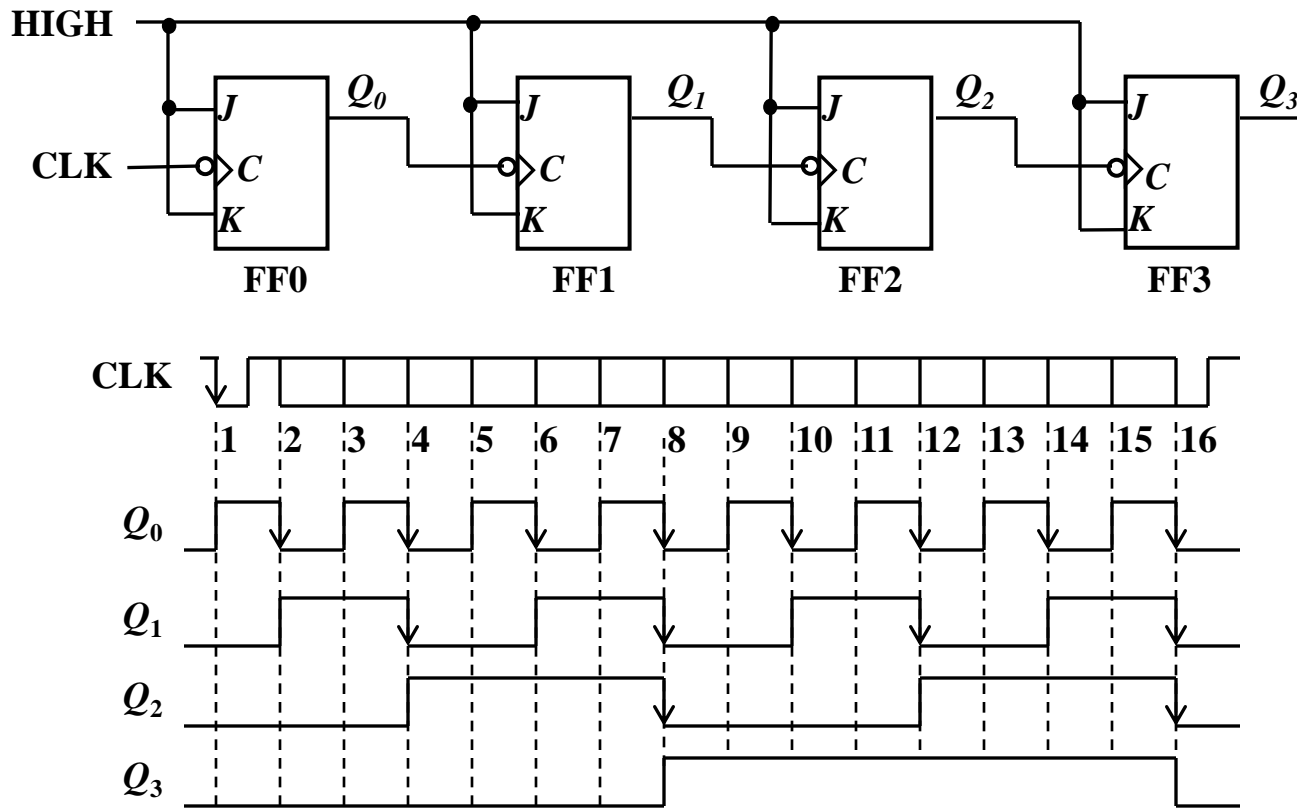- Example: 4-bit ripple binary counter (negative-edge triggered).



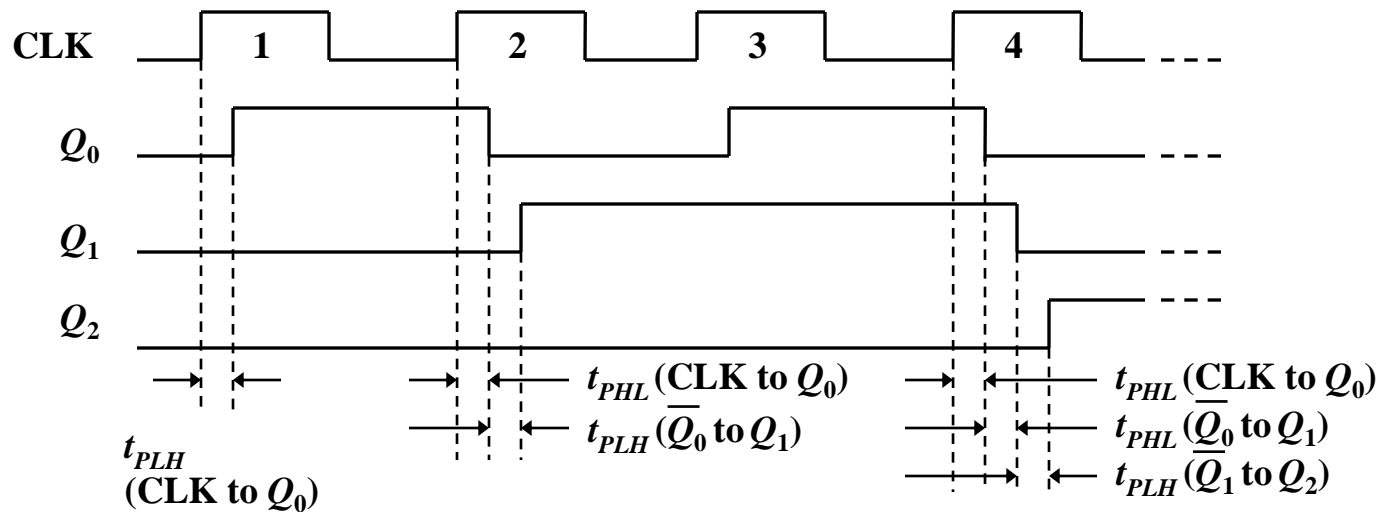
# Asynchronous (Ripple) Counters

- **Propagation delays** in an asynchronous (ripple-clocked) binary counter.
- If the accumulated delay is greater than the clock pulse, some counter states may be misrepresented!




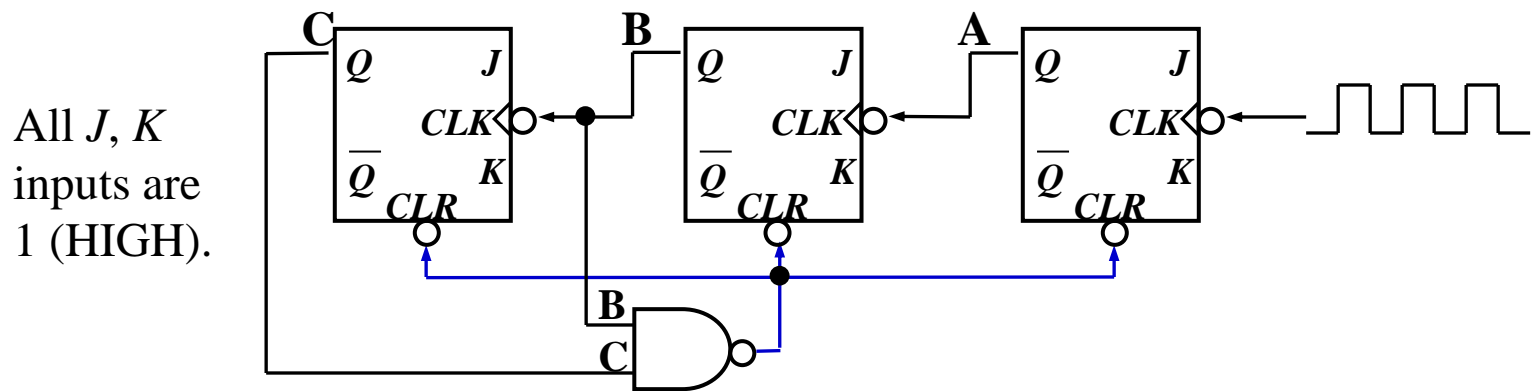
# Asyn. Counters with MOD no. $< 2^n$

- States may be skipped resulting in a **truncated sequence**.
- Technique: force counter to **recycle before going through all of the states** in the binary sequence.
- Example: Given the following circuit, determine the counting sequence (and hence the modulus no.)



# Asyn. Counters with MOD no. $< 2^n$

## ■ Example (cont'd):

 
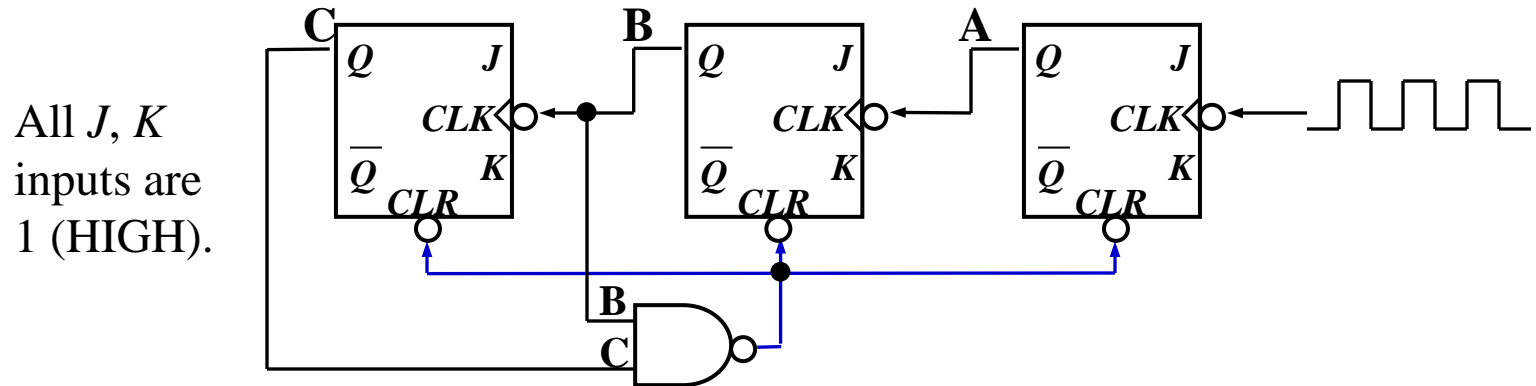


**MOD-6 counter**  
produced by clearing  
(a MOD-8 binary  
counter) when count  
of six (110) occurs.



# Asyn. Counters with MOD no. $< 2^n$

  
- Example (cont'd): Counting sequence of circuit (in **CBA** order).



Counter is a **MOD-6** counter.

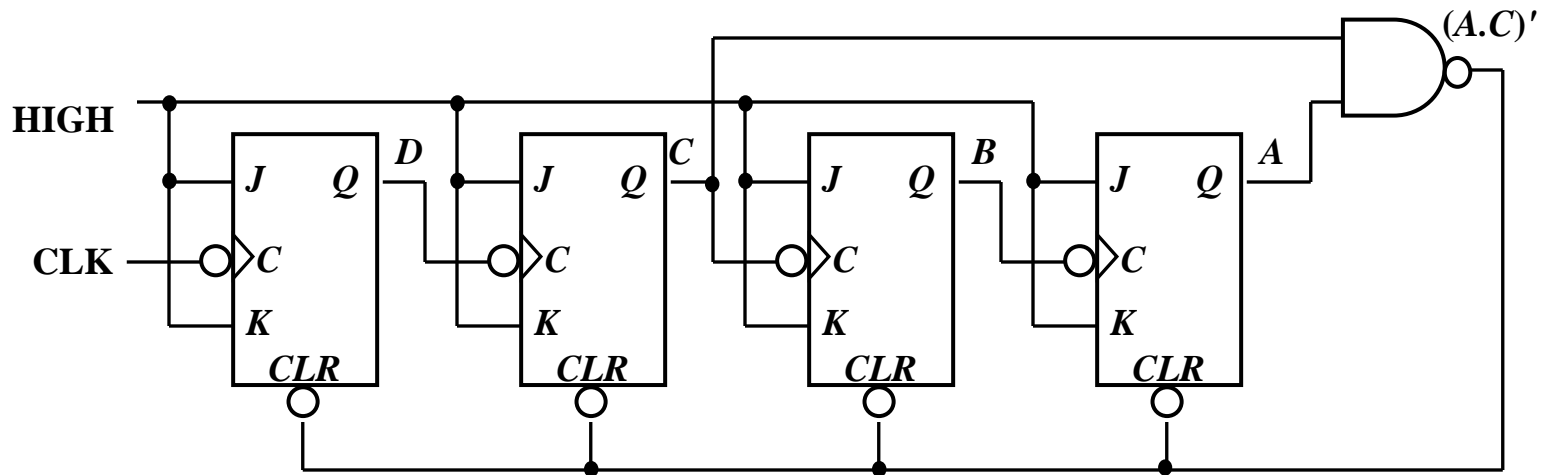
# Asyn. Counters with MOD no. $< 2^n$

- **Decade counters** (or **BCD counters**) are counters with 10 states (modulus-10) in their sequence. They are commonly used in daily life (e.g.: utility meters, odometers, etc.).
- Design an **asynchronous decade counter**.




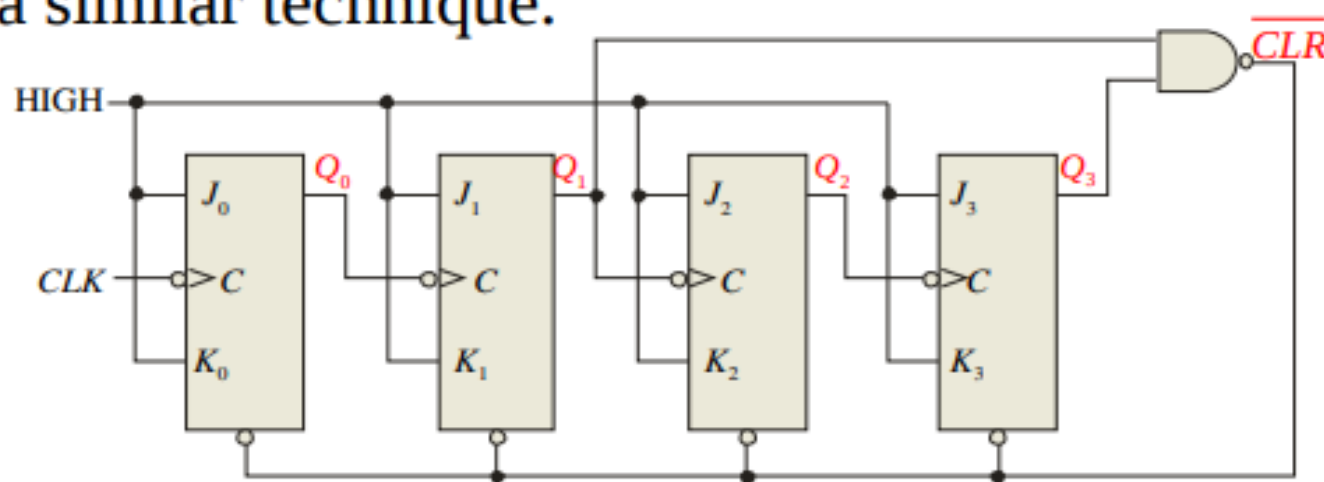
## Asynchronous Decade Counter

This counter uses partial decoding to recycle the count sequence to zero after the 1001 state. The flip-flops are trailing-edge triggered, so clocks are derived from the  $Q$  outputs. Other truncated sequences can be obtained using a similar technique.



 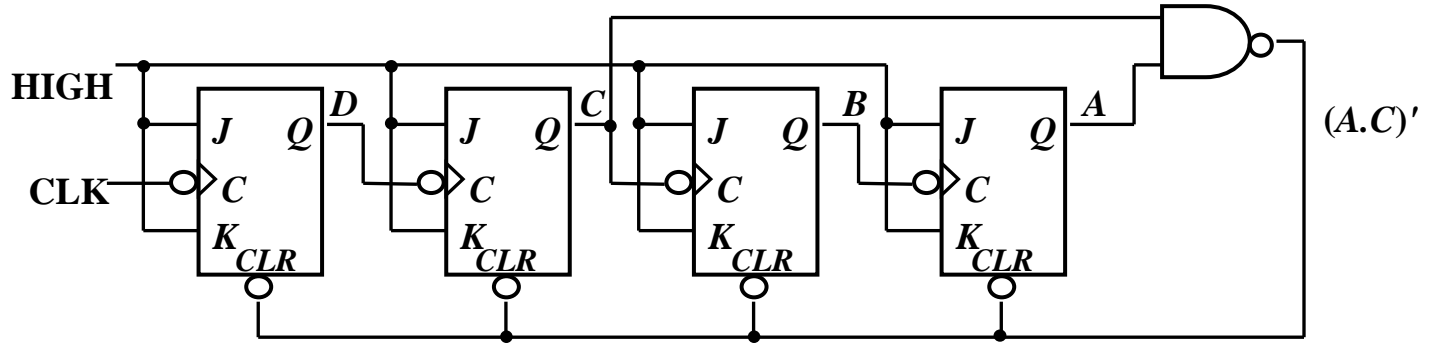
# Asyn. Counters with MOD no. $< 2^n$

- **Asynchronous decade/BCD counter (cont'd).**



 
# Asynchronous Down Counters

- So far we are dealing with *up counters*. **Down counters**, on the other hand, count downward from a maximum value to zero, and repeat.
- Example: A **3-bit binary (MOD-2<sup>3</sup>) down counter**.




3-bit binary  
**up** counter

 

3-bit binary  
**down** counter


# Asynchronous Down Counters

 - Example: A 3-bit binary (MOD-8) down counter.


 
# Synchronous (Parallel) Counters

- **Synchronous (parallel) counters**: the flip-flops are **clocked at the same time** by a common clock pulse.
- We can design these counters using the sequential logic design process.
- Example: **2-bit synchronous binary counter** (using T flip-flops, or JK flip-flops with identical J,K inputs).



Present state		Next state		Flip-flop inputs	
$A_1$	$A_0$	$A_1^+$	$A_0^+$	$TA_1$	$TA_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1


# Synchronous (Parallel) Counters

- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).

Present state		Next state		Flip-flop inputs	
$A_1$	$A_0$	$A_1^+$	$A_0^+$	$TA_1$	$TA_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

$$TA_1 = A_0$$

$$TA_0 = 1$$

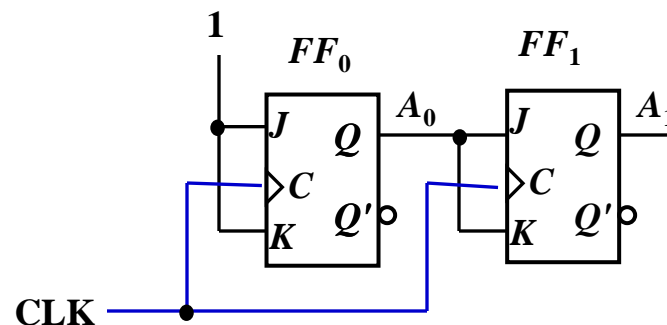



## Synchronous Counters

In a **synchronous counter** all flip-flops are clocked together with a common clock pulse. Synchronous counters overcome the disadvantage of accumulated propagation delays, but generally they require more circuitry to control states changes.

# Synchronous (Parallel) Counters

- Example: **3-bit synchronous binary counter** (using T flip-flops, or JK flip-flops with identical J, K inputs).

Present state			Next state			Flip-flop inputs		
$A_2$	$A_1$	$A_0$	$A_2^+$	$A_1^+$	$A_0^+$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1


# Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (cont'd).

$$TA_2 = A_1.A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

 

# Synchronous (Parallel) Counters


- Example: 4-bit synchronous binary counter

$$TA_3 = A_2 \cdot A_1 \cdot A_0$$


$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$


$$TA_0 = 1$$

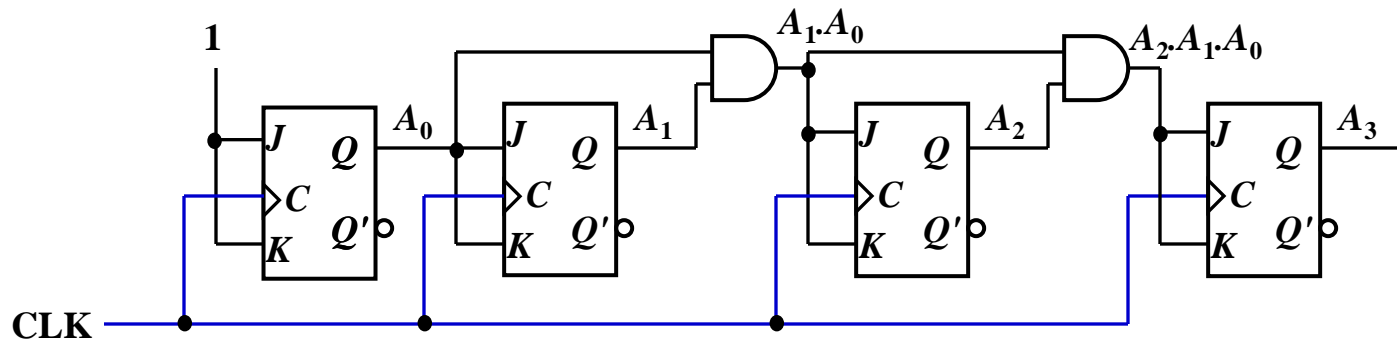

# Synchronous binary Counter

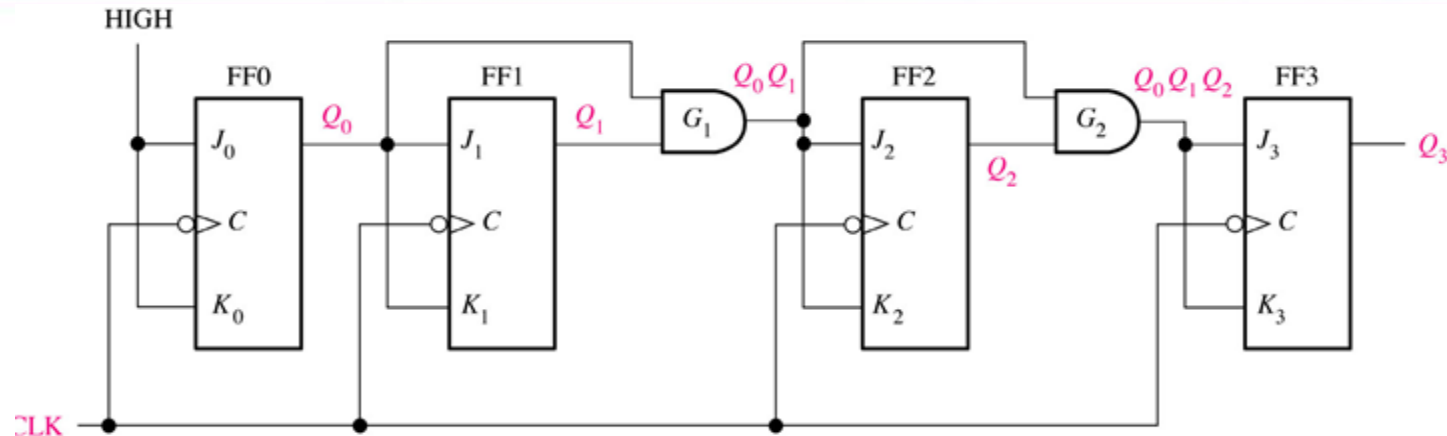

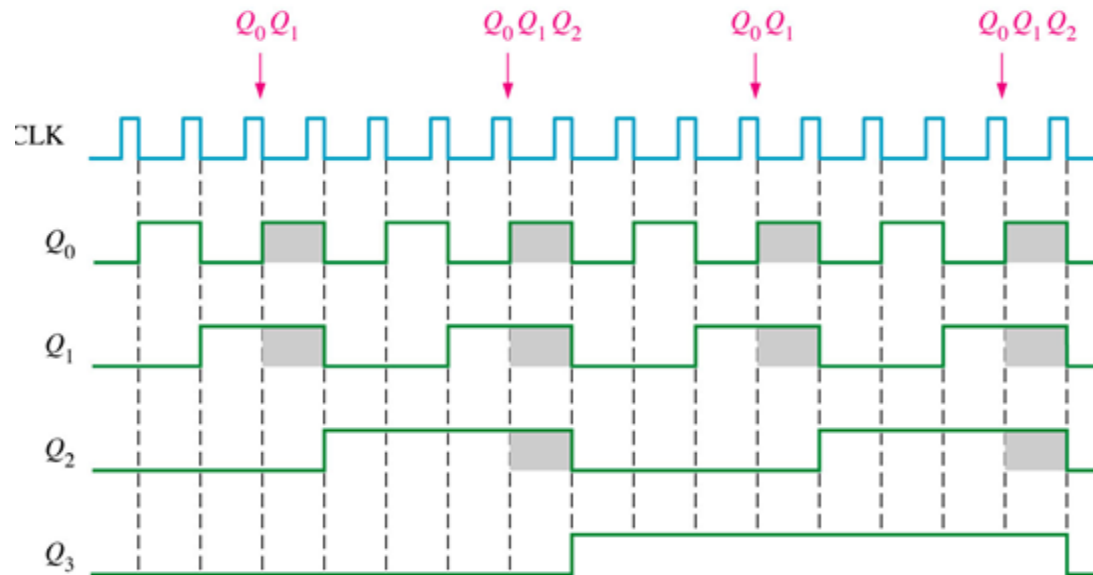(a) A 4-bit synchronous binary counter and timing diagram.



CLK PLUSE	Q3	Q2	Q1	Q0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
16 REPEAT	0	0	0	0

# Synchronous (Parallel) Counters

- Example: Synchronous decade/BCD counter

Clock pulse	$Q_3$	$Q_2$	$Q_1$	$Q_0$
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10 (recycle)	0	0	0	0

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$

$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$

# Synchronous (Parallel) Counters


- Example: Synchronous decade/BCD counter (cont'd).

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$
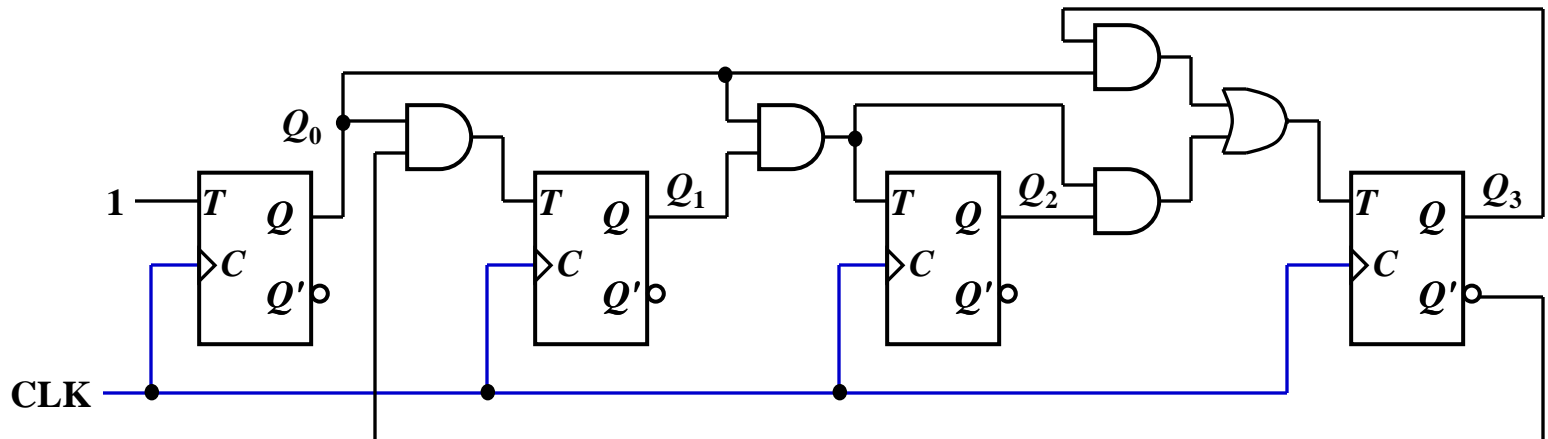
$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$



# Up/Down Synchronous Counters

- **Up/down synchronous counter:** a *bidirectional* counter that is capable of counting either up or down.
- An input (control) line  $Up/\overline{Down}$  (or simply  $Up$ ) specifies the direction of counting.
  - ❖  $Up/\overline{Down} = 1 \rightarrow$  Count upward
  - ❖  $Up/\overline{Down} = 0 \rightarrow$  Count downward



# Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter

Clock pulse	<i>Up</i>	$Q_2$	$Q_1$	$Q_0$	<i>Down</i>
0		0	0	0	
1		0	0	1	
2		0	1	0	
3		0	1	1	
4		1	0	0	
5		1	0	1	
6		1	1	0	
7		1	1	1	

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$

$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$

Up counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0$$

$$TQ_2 = Q_0 \cdot Q_1$$

Down counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0'$$

$$TQ_2 = Q_0' \cdot Q_1'$$


# Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter (cont'd)

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$

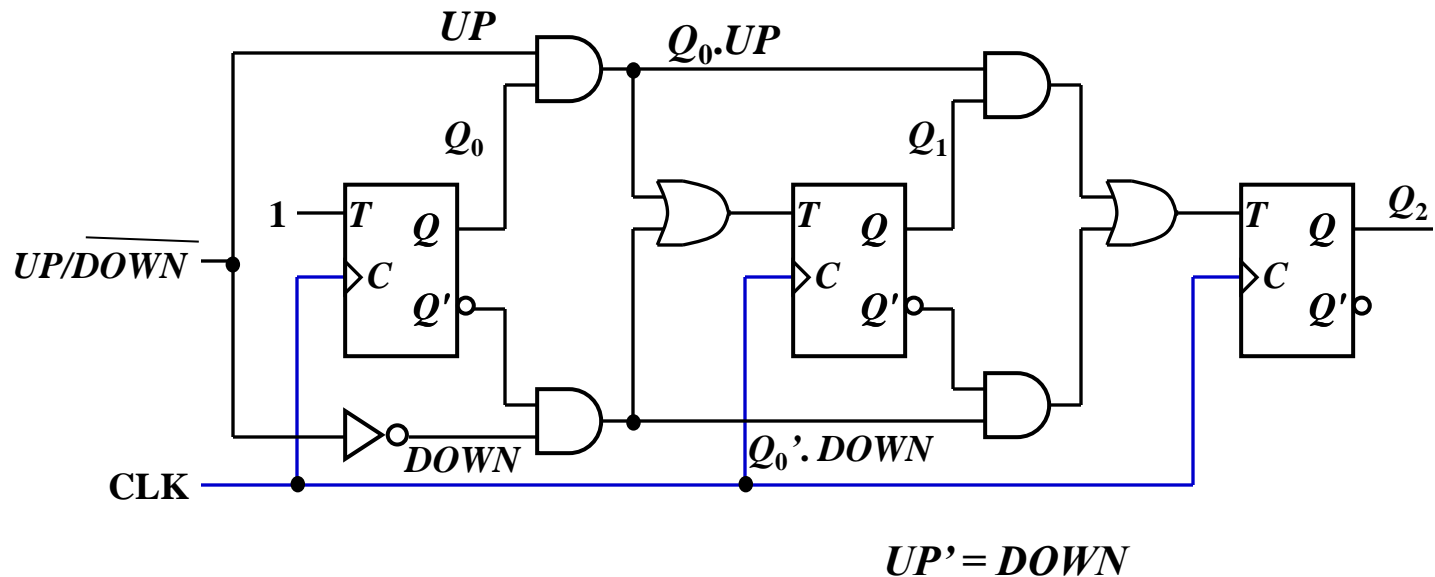
$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$



# Designing Synchronous Counters

- Example: A 3-bit Gray code counter (using JK flip-flops)

1. State diagram:

 

2. Next state table:

Present State			Next State		
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

# Designing Synchronous Counters

- Example: A 3-bit Gray code counter (using JK flip-flops)


## 3. FLIP-FLOP TRANSITION TABLE

Output Transitions $Q_N$ $Q_{N+1}$		Flip-Flop Inputs $J$ $K$	
0	→ 0	0	X
0	→ 1	1	X
1	→ 0	X	1
1	→ 1	X	0

# Designing Synchronous Counters

- Example: A 3-bit Gray code counter (using JK flip-flops)

Output Transitions $Q_N \rightarrow Q_{N+1}$		Flip-Flop Inputs $J \quad K$	
0	→ 0	0	X
0	→ 1	1	X
1	→ 0	X	1
1	→ 1	X	0

 

0
1
3
2
6
7
5
4

Present state			Next state			Flip-flop inputs					
$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$JQ_2$	$KQ_2$	$JQ_1$	$KQ_1$	$JQ_0$	$KQ_0$
0	0	0	0	0	1	0	X	0	X	1	X
1	0	1	0	1	1	0	X	1	X	X	0
3	0	1	0	1	0	0	X	X	0	X	1
2	0	1	1	1	0	1	X	X	0	0	X
6	1	1	1	1	1	X	0	X	0	1	X
7	1	1	1	0	1	X	0	X	1	X	0
5	1	0	1	0	0	X	0	0	X	X	1
4	1	0	0	0	0	X	1	0	X	0	X

# Designing Synchronous Counters

- Example: A 3-bit Gray code counter (using JK flip-flops)

## 4.KARNAUGH MAPS

Each time a flip-flop is clocked, the  $J$  and  $K$  inputs required for that transition are mapped onto a K-map.

An example of the  $J_0$  map is:

$Q_2Q_1$ \ $Q_0$		0	1	
		0	1	
00	1	X	$\bar{Q}_2\bar{Q}_1$	
01	0	X		
11	1	X	$Q_2Q_1$	
10	0	X		

$J_0$  map

# Designing Synchronous Counters

- 3-bit Gray code counter: flip-flop inputs.

## 4. KARNAUGH MAPS

		$Q_1 Q_0$			
		00	01	11	10
$Q_2$	0				1
	1	X	X	X	X

$JQ_2 = Q_1 \cdot Q_0'$

		$Q_1 Q_0$			
		00	01	11	10
$Q_2$	0	X	X	X	X
	1	1			

$KQ_2 = Q_1' \cdot Q_0'$

		$Q_1 Q_0$			
		00	01	11	10
$Q_2$	0		1	X	X
	1			X	X

$JQ_1 = Q_2' \cdot Q_0$

		$Q_1 Q_0$			
		00	01	11	10
$Q_2$	0	X	X		
	1	X	X	1	

$KQ_1 = Q_2 \cdot Q_0$

	$JQ_2$	$KQ_2$	$JQ_1$	$KQ_1$	$JQ_0$	$KQ_0$
0	0	X	0	X	1	X
1	0	X	1	X	X	0
3	0	X	X	0	X	1
2	1	X	X	0	0	X
6	X	0	X	0	1	X
7	X	0	X	1	X	0
5	X	0	0	X	X	1
4	X	1	0	X	0	X

		$Q_1 Q_0$			
		00	01	11	10
$Q_2$	0	1	X	X	
	1		X	X	1

$JQ_0 = Q_2 \cdot Q_1 + Q_2' \cdot Q_1'$   
 $= (Q_2 \oplus Q_1)'$

		$Q_1 Q_0$			
		00	01	11	10
$Q_2$	0	X		1	X
	1	X	1		X

$KQ_0 = Q_2 \cdot Q_1' + Q_2' \cdot Q_1$   
 $= Q_2 \oplus Q_1$

# Designing Synchronous Counters

- 3-bit Gray code counter: logic diagram.


## 5. Logic Expressions for Flip-Flop Inputs

$$\begin{aligned} JQ_2 &= Q_1 \cdot Q_0' \\ KQ_2 &= Q_1' \cdot Q_0' \end{aligned}$$

$$\begin{aligned} JQ_1 &= Q_2' \cdot Q_0 \\ KQ_1 &= Q_2 \cdot Q_0 \end{aligned}$$

$$\begin{aligned} JQ_0 &= (Q_2 \oplus Q_1)' \\ KQ_0 &= Q_2 \oplus Q_1 \end{aligned}$$

## 6. Counter Implementation

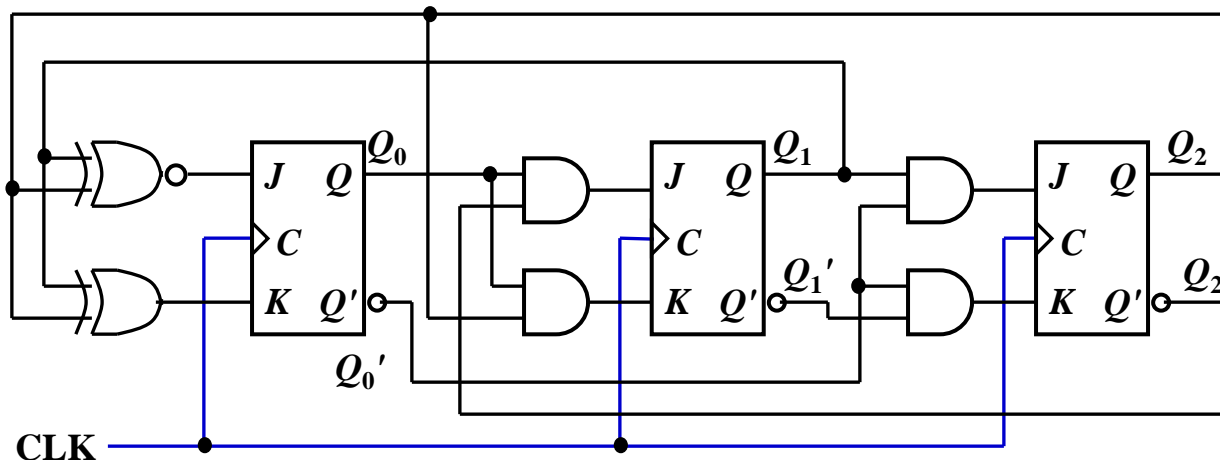



# Synchronous Binary Counter

TABLE 4-10  
Flip-Flop Excitation Tables

(a) JK Flip-Flop

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



## J-K Flip Flop Design of a 4-bit Binary Up Counter

Present state				Next state				Flip-flop inputs							
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_{Q3}$	$K_{Q3}$	$J_{Q2}$	$K_{Q2}$	$J_{Q1}$	$K_{Q1}$	$J_{Q0}$	$K_{Q0}$
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	1	0	1	0	X	0	0	X	1	X	X	1
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
1	0	1	1	1	1	0	0	X	0	1	X	X	1	X	1
1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	X
1	1	0	1	1	1	1	0	X	0	X	0	1	X	X	1
1	1	1	0	1	1	1	1	X	0	X	0	X	0	1	X
1	1	1	1	0	0	0	0	X	1	X	1	X	1	X	1

# Synchronous Binary Counters

## J-K Flip Flop Design of a Binary Up Counter (cont.)

Present state				Next state					
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_{Q3}$	$K_{Q3}$
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	0	X
0	0	1	0	0	0	1	1	0	X
0	0	1	1	0	1	0	0	0	X
0	1	0	0	0	1	0	1	0	X
0	1	0	1	0	1	1	0	0	X
0	1	1	0	0	1	1	1	0	X
0	1	1	1	1	0	0	0	1	X
1	0	0	0	1	0	0	1	X	0
1	0	0	1	1	0	1	0	X	0
1	0	1	0	1	0	1	1	X	0
1	0	1	1	1	1	0	0	X	0
1	1	0	0	1	1	0	1	X	0
1	1	0	1	1	1	1	0	X	0
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

  

# Synchronous Binary Counters

## J-K Flip Flop Design of a Binary Up Counter (cont.)

Present state				Next state				Flip-flop	
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_{Q2}$	$K_{Q2}$
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	0	X
0	0	1	0	0	0	1	1	0	X
0	0	1	1	0	1	0	0	1	X
0	1	0	0	0	1	0	1	X	0
0	1	0	1	0	1	1	0	X	0
0	1	1	0	0	1	1	1	X	0
0	1	1	1	1	0	0	0	X	1
1	0	0	0	1	0	0	1	0	X
1	0	0	1	1	0	1	0	0	X
1	0	1	0	1	0	1	1	0	X
1	0	1	1	1	1	0	0	1	X
1	1	0	0	1	1	0	1	X	0
1	1	0	1	1	1	1	0	X	0
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

		1	
X	X	X	X
X	X	X	X
		1	

$$J_{Q2} = Q_0 Q_1$$

X	X	X	X
		1	
		1	
X	X	X	X

$$K_{Q2} = Q_0 Q_1$$

# Synchronous Binary Counters

## J-K Flip Flop Design of a Binary Up Counter (cont.)

Present state				Next state				p inputs	
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_{Q1}$	$K_{Q1}$
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	1	X
0	0	1	0	0	0	1	1	X	0
0	0	1	1	0	1	0	0	X	1
0	1	0	0	0	1	0	1	0	X
0	1	0	1	0	1	1	0	1	X
0	1	1	0	0	1	1	1	X	0
0	1	1	1	1	0	0	0	X	1
1	0	0	0	1	0	0	1	0	X
1	0	0	1	1	0	1	0	1	X
1	0	1	0	1	0	1	1	X	0
1	0	1	1	1	1	0	0	X	1
1	1	0	0	1	1	0	1	0	X
1	1	0	1	1	1	1	0	1	X
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

		1	X	X
		1	X	X
		1	X	X
		1	X	X


$$J_{Q1} = Q_0$$

X	X	1	
X	X	1	
X	X	1	
X	X	1	

$$K_{Q1} = Q_0$$

# Synchronous Binary Counters
 
## J-K Flip Flop Design of a Binary Up Counter (cont.)



$$J_{Q_0} = 1$$

$$K_{Q_0} = 1$$

$$J_{Q_1} = Q_0$$

$$K_{Q_1} = Q_0$$

$$J_{Q_2} = Q_0 Q_1$$

$$K_{Q_2} = Q_0 Q_1$$

$$J_{Q_3} = Q_0 Q_1 Q_2$$

$$K_{Q_3} = Q_0 Q_1 Q_2$$

# Synchronous (Parallel) Counters

- Example: **3-bit synchronous binary counter** (using T flip-flops, or JK flip-flops with identical J, K inputs).

$A_1$   $A_0$   
 00 01 11 10  
 $A_2$  0  
 1

		1	
		1	

$TA_2 = A_1 \cdot A_0$

Present state			Next state			Flip-flop inputs		
$A_2$	$A_1$	$A_0$	$A_2^+$	$A_1^+$	$A_0^+$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

$A_1$

		1	
		1	

$A_0$

$TA_2 = A_1 \cdot A_0$

$A_1$

	1	1	
	1	1	

$A_0$

$TA_1 = A_0$

$A_1$


1	1	1	1
1	1	1	1

$A_0$


$TA_0 = 1$

# Synchronous Binary Counters
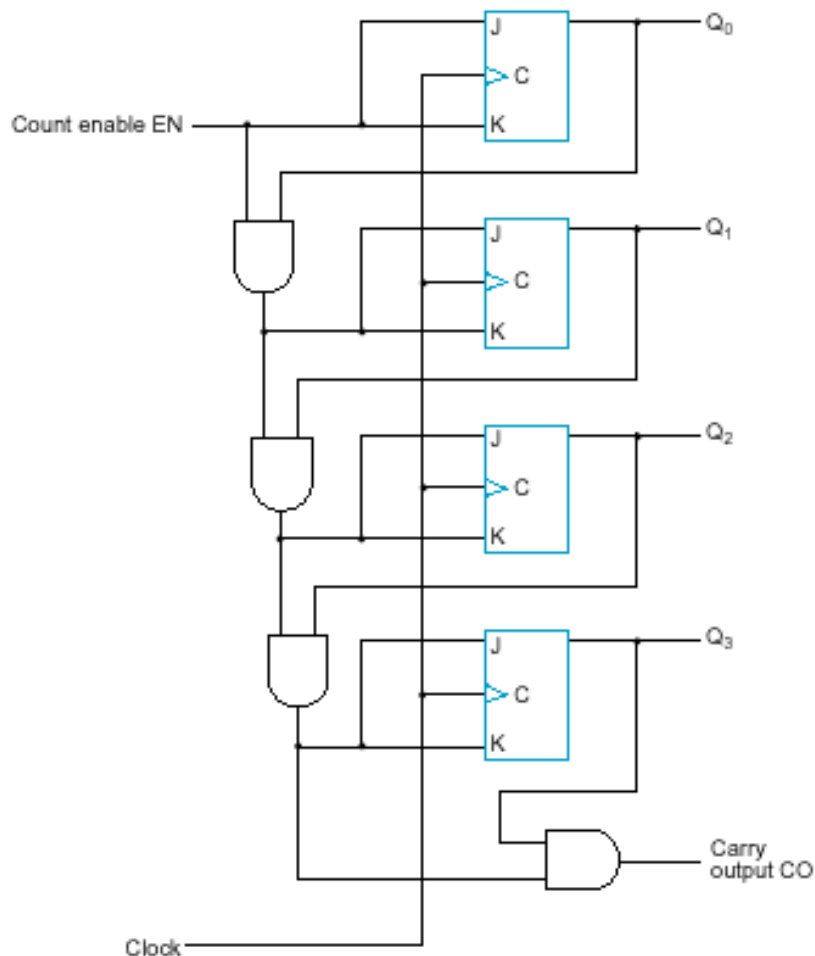
## J-K Flip Flop Design of a Binary Up Counter with EN and CO



(a) Logic diagram

 

(b) Symbol

EN = enable control signal,  
when 0 counter remains in  
the same state, when 1 it  
counts

CO = carry output signal,  
used to extend the counter  
to more stages

$$J_{Q0} = 1 \cdot EN$$

$$K_{Q0} = 1 \cdot EN$$

$$J_{Q1} = Q_0 \cdot EN$$

$$K_{Q1} = Q_0 \cdot EN$$

$$J_{Q2} = Q_0 Q_1 \cdot EN$$

$$K_{Q2} = Q_0 Q_1 \cdot EN$$


$$J_{Q3} = Q_0 Q_1 Q_2 \cdot EN$$

$$K_{Q3} = Q_0 Q_1 Q_2 \cdot EN$$

$$CO = Q_0 Q_1 Q_2 Q_3 \cdot EN$$

# Counter

*A four-bit synchronous "up" counter*

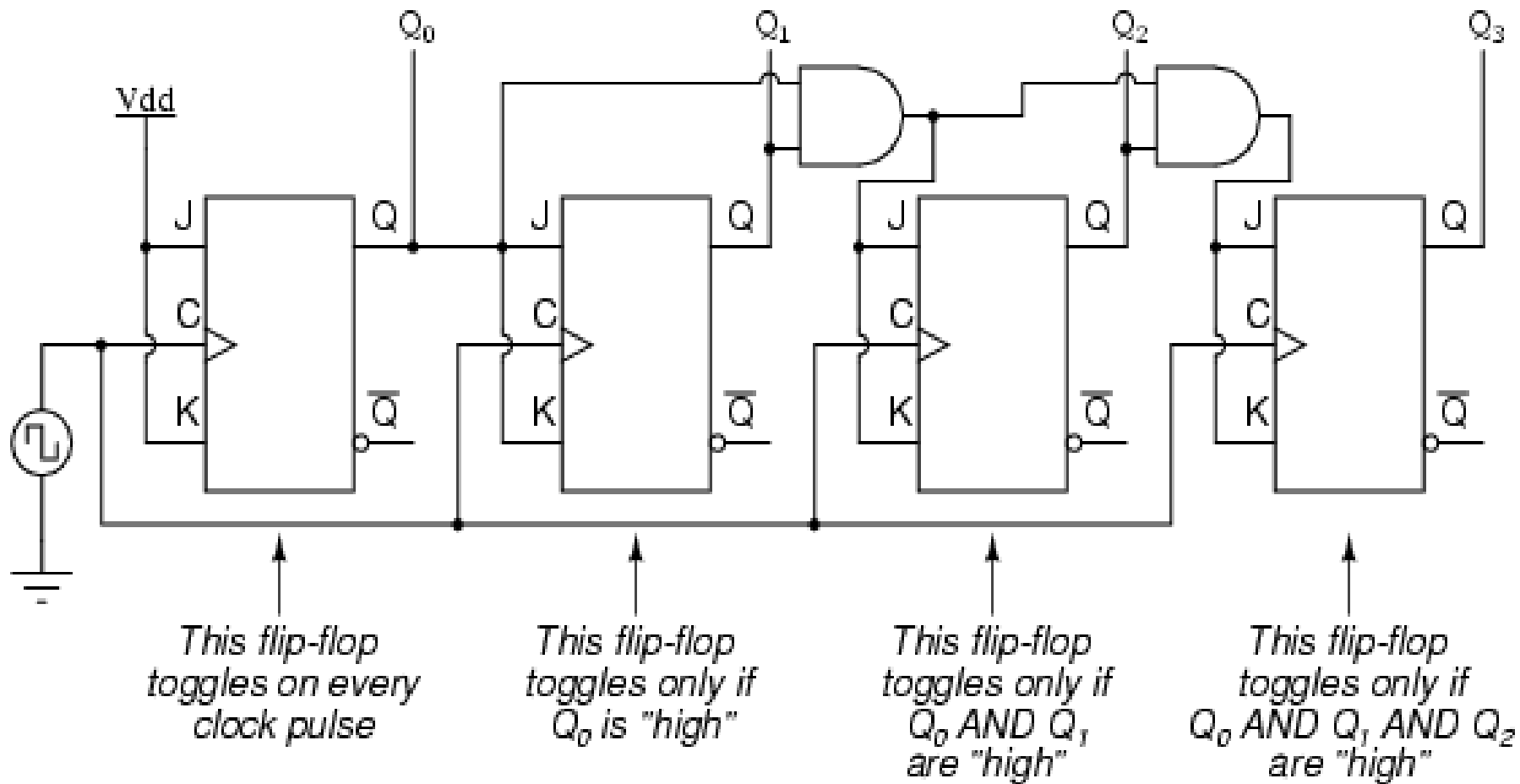



A small rectangular image showing a close-up of a circuit board with various components and labels like 'P1', 'P2', and 'VEA'.

# Summary

## Module II (10 Hours)


Sequential circuit - Clocking, Flip flops - SR – JK- D -T flip flops, Counters - Synchronous and asynchronous counters - UP/DOWN counters, Registers - Serial in serial out - Serial in parallel out - Parallel in serial out - Parallel in parallel out registers

# Introduction: Registers

- An  $n$ -bit register has a group of  $n$  flip-flops and some logic gates and is capable of storing  $n$  bits of information.
- The flip-flops store the information while the gates control when and how new information is transferred into the register.
- Some functions of register:
  - ❖ retrieve data from register
  - ❖ store/load new data into register (serial or parallel)
  - ❖ shift the data within register (left or right)
 
# Simple Registers

- No external gates.
- Example: A **4-bit register**. A new 4-bit data is loaded every clock cycle.




# Registers With Parallel Load

- Instead of loading the register at every clock pulse, we may want to control when to load.
- *Loading* a register: transfer new information into the register. Requires a *load* control input.
- *Parallel loading*: all bits are loaded simultaneously.
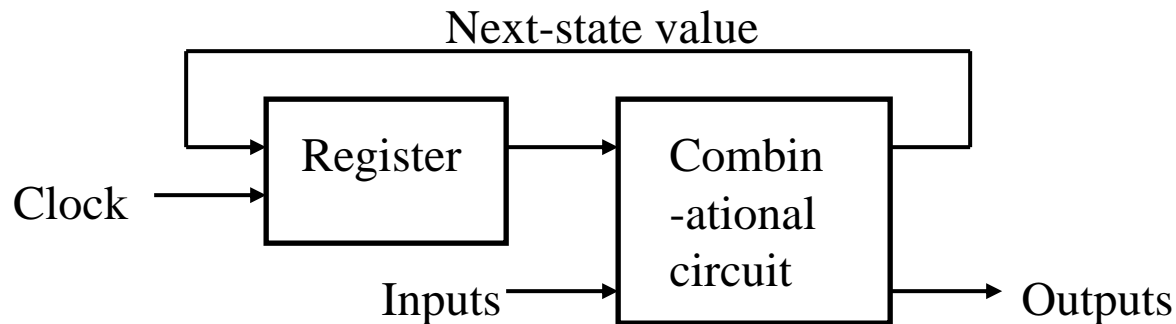
# Using Registers to implement Sequential Circuits

- A sequential circuit may consist of a *register* (memory) and a *combinational circuit*.




- The **external inputs** and **present states of the register** determine the **next states of the register** and the **external outputs**, through the combinational circuit.

# Shift Registers


- Another function of a register, besides storage, is to provide for *data movements*.
- Each *stage* (flip-flop) in a shift register represents one bit of *storage*, and the *shifting capability* of a register permits the movement of data from stage to stage within the register, or into or out of the register upon application of clock pulses.
 
# Shift Registers


- Basic data movement in shift registers (four bits are used for illustration).




**(a) Serial in/shift right/serial out**

 


**(b) Serial in/shift left/serial out**

 


**(c) Parallel in/serial out**

 


**(d) Serial in/parallel out**

 

**(e) Parallel in / parallel out**

 


**(f) Rotate right**

 


**(g) Rotate left**

# Shift Register


Serial In / Serial Out  
Left-to-Right

 


Serial In / Serial Out  
Right-to-Left

 

Parallel In / Serial Out

 



Serial In / Parallel Out

 



 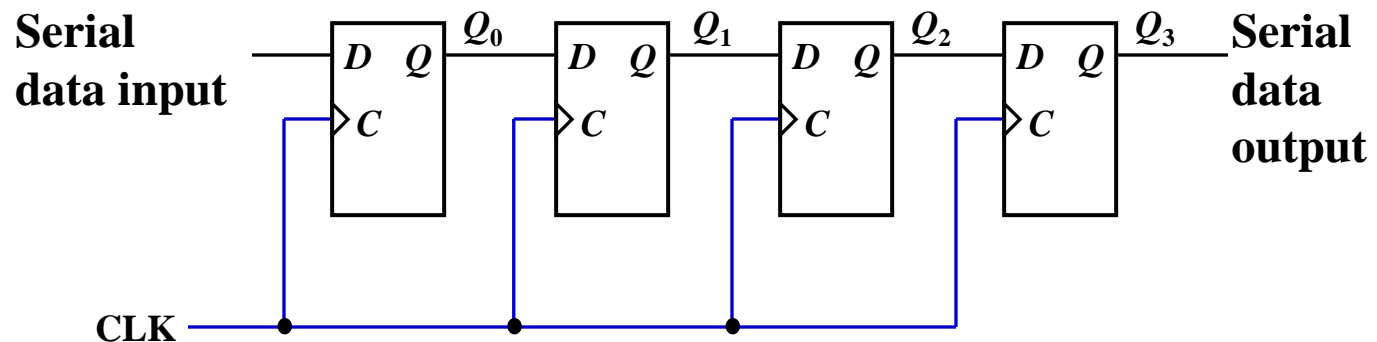
# Serial In/Serial Out Shift Registers

- **Accepts data serially** – one bit at a time – and also produces output serially.


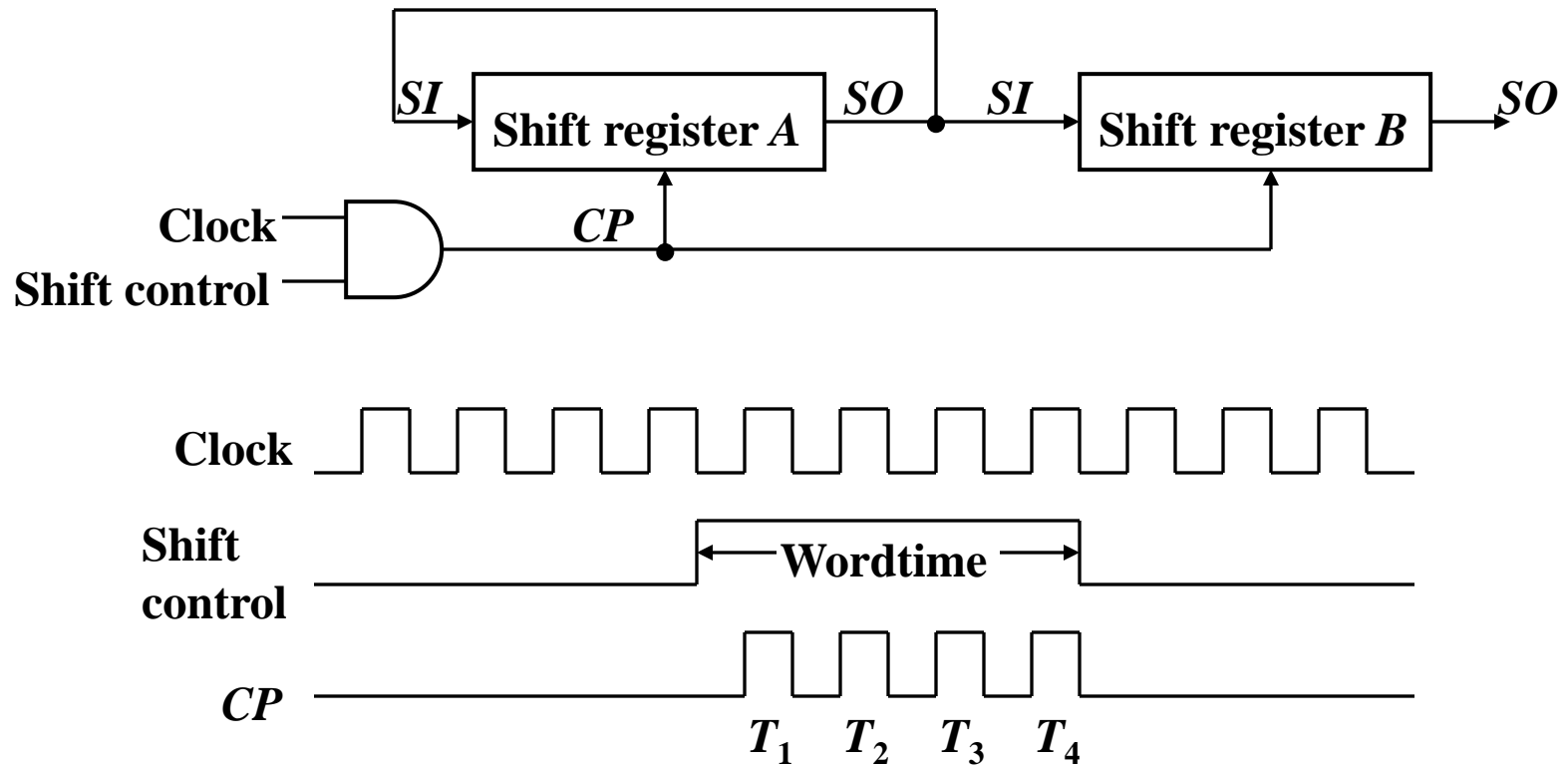
# Serial In/Serial Out Shift Registers

- Application: Serial transfer of data from one register to another.



# Serial In/Serial Out Shift Registers

- Serial-transfer example.


Timing Pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After $T_1$	1 1 0 1	1 0 0 1	1
After $T_2$	1 1 1 0	1 1 0 0	0
After $T_3$	0 1 1 1	0 1 1 0	0
After $T_4$	1 0 1 1	1 0 1 1	1

# Summary
 
## Serial-in/Serial out Shift Register

Shift registers are available in IC form or can be constructed from discrete flip-flops as is shown here with a **five-bit serial-in serial-out register**.

Each clock pulse will move an input bit to the next flip-flop. For example, a 1 is shown as it moves across.




# Summary

## Basic System Functions

One type of storage function is the shift register, that moves and stores data each time it is clocked.

Serial bits  
on input line

0101 →

 

Initially the register contains only invalid data or all zeros as shown here.

010 →




First bit (1) is shifted serially into the register.

01 →




Second bit (0) is shifted serially into register and first bit is shifted right.

0 →

 

Third bit (1) is shifted into register and the first and second bits are shifted right.




→

 

Fourth bit (0) is shifted into register and the first, second, and third bits are shifted right. The register now stores all four bits and is full.

 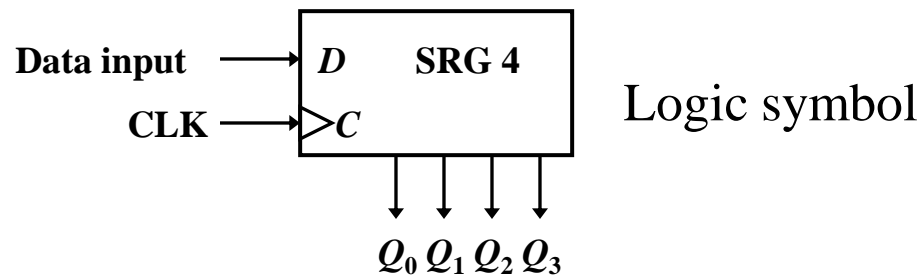 
# Serial In/Parallel Out Shift Registers

- Accepts data serially.
- Outputs of all stages are available simultaneously.



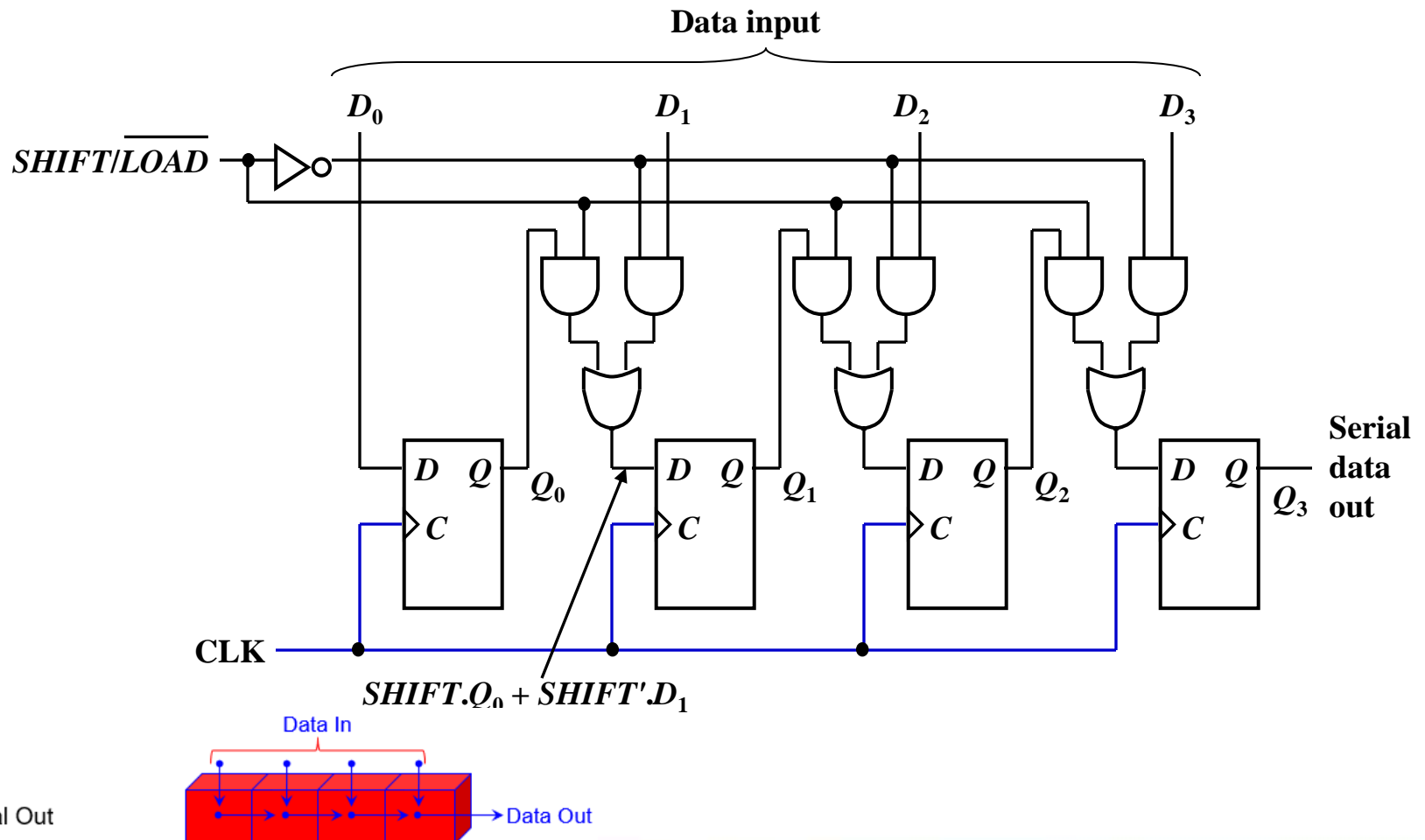
# Parallel In/Serial Out Shift Registers

- Bits are entered simultaneously, but **output is serial**.


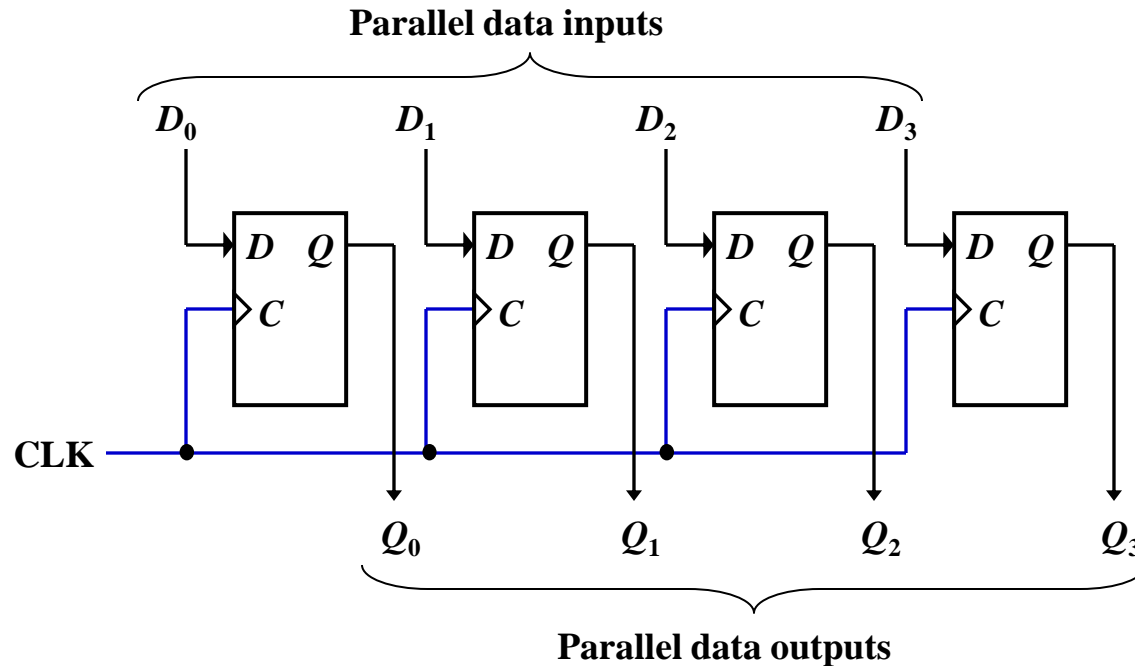
# Parallel In/Parallel Out Shift Registers

- Simultaneous input and output of all data bits.





# Shift Register Counters


- **Shift register counter**: a shift register with the serial output connected back to the serial input.
- They are classified **as counters because they give a specified sequence of states**.
- Two common types: the *Johnson counter* and the *Ring counter*.

# Ring Counters

- One flip-flop (stage) for each state in the sequence.
- The output of the last stage is connected to the D input of the first stage.
- An  $n$ -bit ring counter cycles through  $n$  states.
- No decoding gates are required, as there is an output that corresponds to every state the counter is in.

# Ring Counters

- Example: A 6-bit (MOD-6) ring counter.

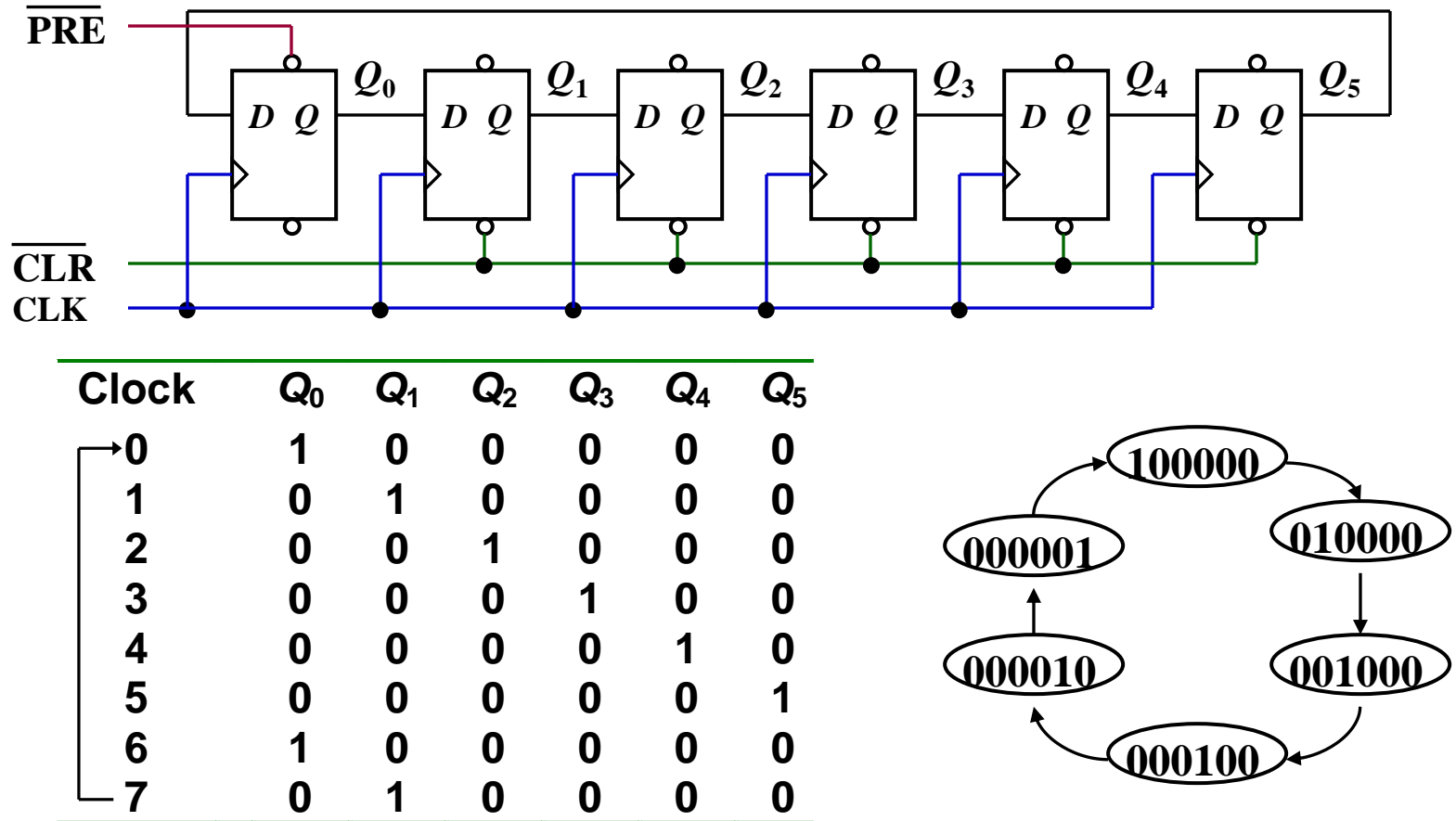


# Johnson Counters

- The complement of the output of the last stage is connected back to the D input of the first stage.
- Also called the *twisted-ring counter*.
- Require fewer flip-flops than ring counters but more flip-flops than binary counters.
- An  $n$ -bit Johnson counter cycles through  $2n$  states.
- Require more decoding circuitry than ring counter but less than binary counters.

# Johnson Counters

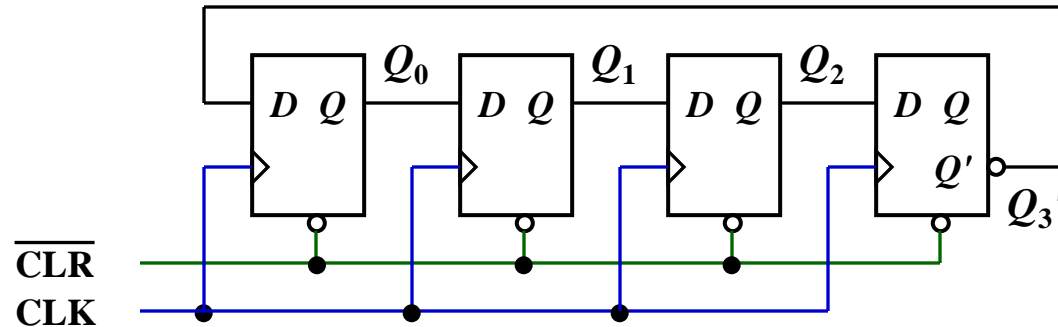- Example: A 4-bit (MOD-8) Johnson counter.



Clock	$Q_0$	$Q_1$	$Q_2$	$Q_3$
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

